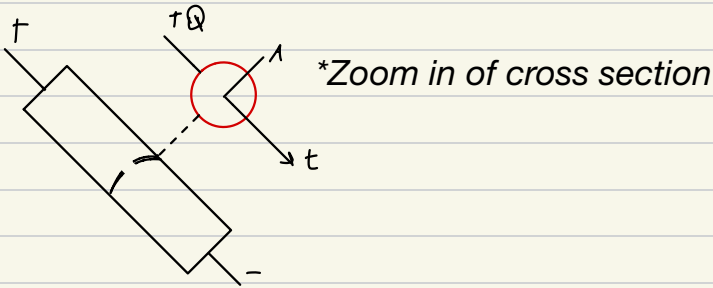



Current, Power, and Resistance

Electric Current (I) is the rate of the flow of charge (Q) through a cross section (A) in a unit of time (t)



$$I = Q/t$$

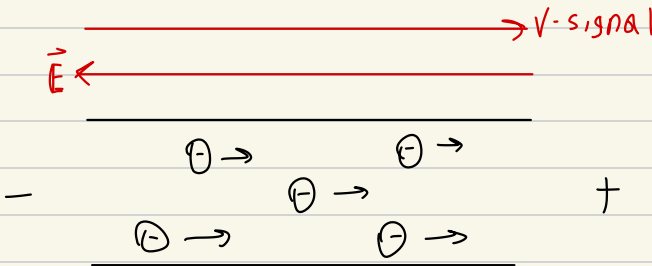- One Ampere (A) is charge flowing at the rate of one Coulomb per second (C/s)




- Electrons “drift” in wire - Slow Drift velocity (Ex. 0.000002 m/s)
- Thermal velocity - (Fast but “random”) (Ex. 1.57 million m/s)
 - Collision velocities
- The electrons bounce around by colliding with different molecules
- E-Field goes back, and since electron, E-Force is to the right

Ex. Electric current in a wire is 6A. How many electrons flow past a given point in a time of 3 seconds.

$$\begin{aligned} I &= 6 \text{ A} & 6 &= \frac{q}{3} & \frac{18}{1.6 \times 10^{-19}} &= \boxed{1125 \times 10^{20} e^-} \\ I &= \frac{q}{t} & q &= 18 \text{ C} \end{aligned}$$

Conventional Current:

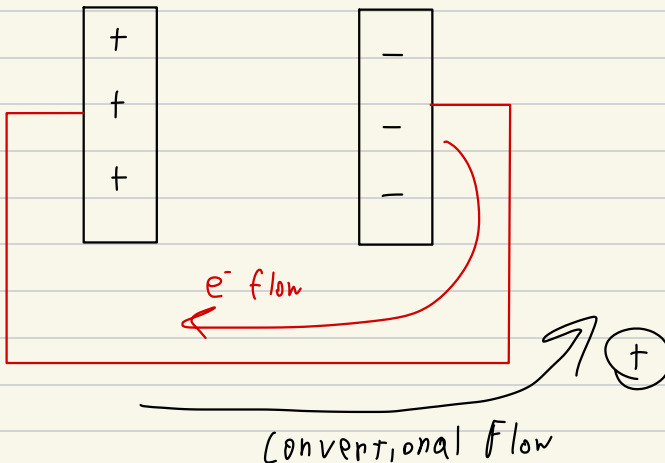- Imagine a capacitor (two conducting plates with opposite charge) that is allowed to discharge
- Electron Flow - The direction of electron flow from - to +
- Conventional Current - the motion of +q from - to +



- Electric fields and potential are defined in terms of +q, so we will assume conventional current (even if electron flow is actual flow)

Electromotive Force:


- A source of Electromotive force (emf) is a device that used chemical, mechanical or other energy to provide the potential difference necessary for electric current.
 - Ex. Power lines, battery, wind generator

Electrical Circuit Symbols:

- Electrical Circuits: often contain one or more resistors grouped together and attach to an energy source, such as a battery




Ground

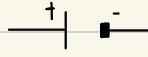


Battery



Resistor

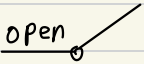

open

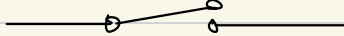

light bulb

Electric Resistance:

Suppose we apply a constant potential difference of 4V to the ends of geometrically similar rods of, say: steel, copper, and glass

- Materials have an electric resistance (R) property

Ohm's Law:

- Current I through a given conductor is directly proportional to the potential difference V between its end points

$$I \propto \Delta V$$

$$I = \frac{\Delta V}{R}; \Delta V = IR; R = \frac{\Delta V}{I}$$

Ex2. When a 3V battery is connected to a light, a current of 6mA is observed. What is the resistance of the light filament

$$R = \Delta V / I = 3 / .006 = 500 \Omega$$
$$\Omega = \frac{V}{A}$$

Factors Affecting Resistance:

- The length L of the material. Longer materials have greater resistance

$$\frac{1L}{1\Omega} \qquad \frac{2L}{2\Omega}$$

- Cross-sectional area A of the material. Larger areas offer LESS resistance
- The temperature T of the material. The higher temperatures usually result in higher resistance
- Kind of material. Iron has more electrical resistance than a geometrically similar copper conductor

Resistivity of a Material:

- The resistivity (ρ) is a property of a material that determines its electrical resistance R.

$$R = \rho \frac{L}{A} \quad \text{or} \quad \rho = \frac{RA}{L}$$

Ex. What length L of copper wire is required to produce a 4mOMEGA resistor? Assume the diameter of the wire is 1mm and that the resistivity ρ of copper is 1.72×10^{-8} OMEGA x m.

$$A = \frac{\pi D^2}{4} = \frac{\pi (.001)^2}{4} = 7.85 \times 10^{-7} \text{ m}^2$$

$$L = \frac{RA}{\rho} = \frac{(.004)(7.85 \times 10^{-7})}{1.72 \times 10^{-8}} = .183 \text{ m}$$

Temperature Coefficient:

For most materials, the resistance R changes in proportion to the initial resistance R_0 and to the change in temperature (ΔT).

$$\Delta R = \alpha R_0 \Delta T \quad \text{or} \quad \rho(T) = \rho_0 + \rho_0 \alpha \Delta T$$

• Ex.

- The resistance of a copper wire is $4\text{m}\Omega$ at 20°C . What will be its resistance if heated to 80°C . $\alpha = .004 / ^\circ\text{C}$

$$R_0 = 4\text{m}\Omega \quad \Delta T = 80^\circ\text{C} - 20^\circ\text{C} = 60^\circ\text{C}$$

$$\Delta R = \alpha R_0 \Delta T; \Delta R = (.004 / ^\circ\text{C}) (4\text{m}\Omega) (60^\circ\text{C})$$

$$\Delta R = 1.03\text{m}\Omega \quad R = R_0 + \Delta R$$

$$R = 4\text{m}\Omega + 1.03\text{m}\Omega$$

Electric Power:

• Electric power P is the rate at which electric energy is expended, or work per unit of time

- Work = $q(\text{potential difference})$

$$P = \frac{W}{t} = \frac{q\Delta V}{t} \quad \& \quad I = \frac{q}{t}$$

$$\Delta V = IR$$

$$P = \Delta V(I)$$

$$P = I^2 R$$

$$P = \frac{\Delta V^2}{R}$$

A power is rated at a 9A when used with a circuit that provides 120-V. What power is used in operating this tool?

$$P = \Delta V I = (120)(9) = 1080 \text{ W}$$

A 500W heater draws a current of 10A. What is resistance?

$$R = P/I^2 = \frac{500}{10^2} = 5 \Omega$$

How much energy does a 60W bulb consume in a week if it stays lighted for 12 hrs a day.

$$P = 60 \text{ W} \quad t = 302400 \text{ s}$$

$$P = E/t \rightarrow E = P \times t = 18144000 \text{ J}$$

We can express the power of the light bulb in KiloWatts instead of Watts

- W $\rightarrow$ kW
- Divide the power in watts by 1000

$$P = \frac{60}{1000} = .06 \text{ kW}$$

$$t = 12 \times 7 = 84 \text{ hrs}$$


$$E = P \times t = 5.04 \text{ kWh}$$

$$\begin{array}{lll} I = Q/t & I = \Delta V/R & R = \Delta V/I \\ A = 1^C/1s & \Delta V = IR & 10hm = 10^3\Omega/1A \end{array}$$

More Circuits (Resistors and Current):

Current (I):

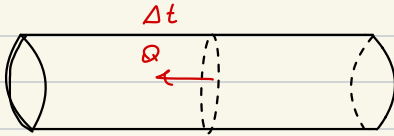- Defined as the rate of flow of charge past a cross section of a wire



$$I = \frac{\Delta Q}{\Delta t}$$

$$\lim_{\Delta t \rightarrow 0} I = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt}$$

$$I \propto \frac{1}{R}$$

$$I \propto \Delta V$$

$$\therefore I = \Delta V / R$$

$$\Delta x = v_d \Delta t$$

$$V = A \Delta x = A v_d \Delta t$$

$$\rightarrow V = v_d / \mu_{me}$$

$$Q = q_e n V$$

n = Electron per unit volume

A = Cross section Area


$$Q = q_e n A v_d \Delta t$$

$$I = \frac{Q}{\Delta t} = n q_e v_d A$$

- The battery:

- Provides/Gives potential energy to the charges as they move through

The Resistor:

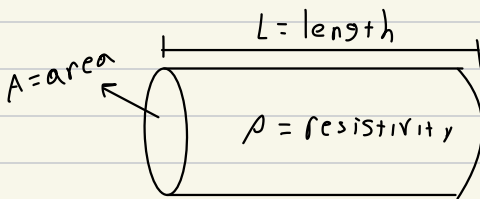

$$R (\Omega)$$

ohms

$$I \propto A$$

$$I = \frac{\Delta V}{R}$$

$$\therefore R \propto \frac{1}{A}, R \propto l$$

$$R = \rho \frac{l}{A}$$


ρ = resistivity

Conductivity $\rightarrow \sigma = 1/\rho$

- Electrons don't just smoothly pass through a wire
- The electrons collide with the electrons in the copper atom (held on the outside), and have tons of collisions with them, 'zig-zagging' their way through the wire
- The **Drift Velocity** (mm/s) is the average vector the electrons follow

Series Circuits:

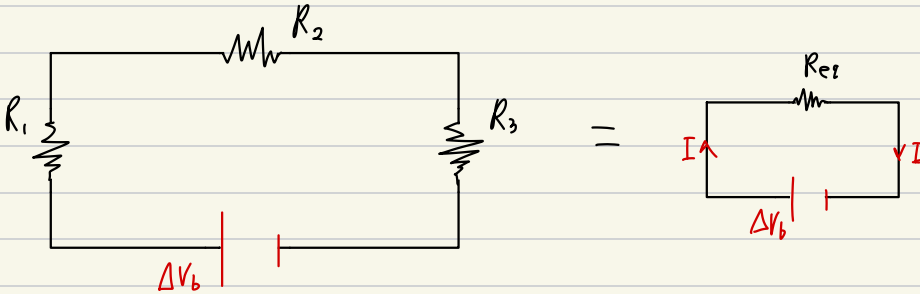Consider 3 resistors R_1 , R_2 , R_3 . We connect them in a series with a power supply (ΔV_b)



- Series = combination of resistors in a single loop circuit with the same current flowing through each element

$$I_1 = I_2 = I_3 = I$$


- In this current loop, the potential rise across the battery = sum of potential drop across the resistors

$$\Delta V_b = \Delta V_1 + \Delta V_2 + \Delta V_3$$

Ohm's: $\Delta V_1 = I_1 R_1$, $\Delta V_2 = I_2 R_2$, $\Delta V_3 = I_3 R_3$

$$\cancel{I} R_{eq} = \cancel{I} R_1 + \cancel{I} R_2 + \cancel{I} R_3 \rightarrow \cancel{I} R_1 + \cancel{I} R_2 + \cancel{I} R_3$$
$$R_{eq} = R_1 + R_2 + R_3$$

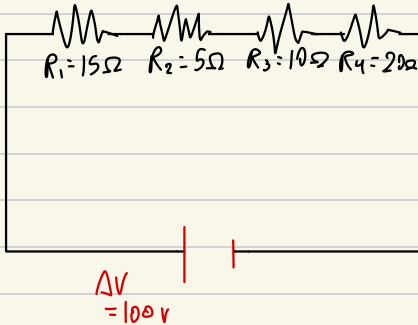Four resistors 15, 5, 10 and 20 are connected in a Series with a 100V. Find the equivalent resistance, total current in the circuit and the current through and potential difference across each resistor in the combination.



$$R_{eq} = R_1 + R_2 + R_3 + R_4$$

$$R_{eq} = 50\Omega$$

$$\Delta V_b = I_{tot} R_{eq}$$

$$100 = 50(I_{tot})$$

$$I_{tot} = 2\text{A}$$

$$I_{tot} = I_1 = I_2 \dots = I_4 = 2\text{A}$$

$$\Delta V_1 = I_1 R_1 = 30\text{V}$$


$$\Delta V_2 = I_2 R_2 = 10\text{V}$$

$$\Delta V_3 = 20\text{V}$$

$$\Delta V_4 = 40\text{V}$$

Parallel Circuits

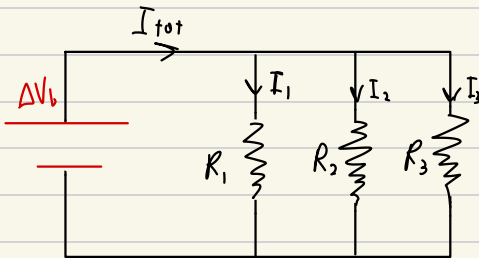- Circuit elements are connected such that they have the same potential difference across them.



$$\Delta V_1 = \Delta V_2 = \Delta V_3 = \Delta V_b$$


$$I_{tot} = I_1 + I_2 + I_3$$

$$I_{tot} = \Delta V_b / R_{eq}$$

$$\Delta V_b / R_{eq} = \Delta V_b / R_1 + \Delta V_b / R_2 + \Delta V_b / R_3$$

$$1/R_{eq} = 1/R_1 + \dots + 1/R_3$$

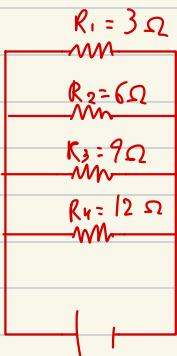Ex. 4 resistors, 3, 6, 9, 12 are connected in parallel across 36V battery. Find Eq Resistance and total current drawn. What is potential diff across and through each resistor?



$$R_{eq} = (1/3 + 1/6 + 1/9 + 1/12)^{-1} = 1.44 \Omega$$

$$\Delta V_b = I_{tot} R_{eq}$$

$$I_{tot} = 25 A$$

$$\Delta V_1 = \dots \Delta V_4 = 36 V$$

$$\Delta V_1 = I_1 R_1 \rightarrow I_1 = 12 A$$




$$I_2 = 6 A$$


$$I_3 = 4 A$$

$$I_4 = 3 A$$

Complex Series and Circuits

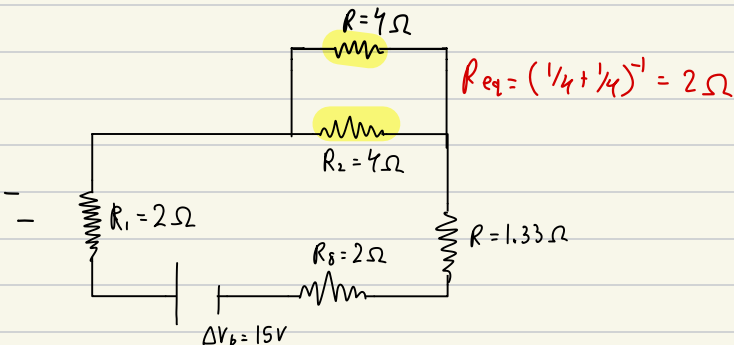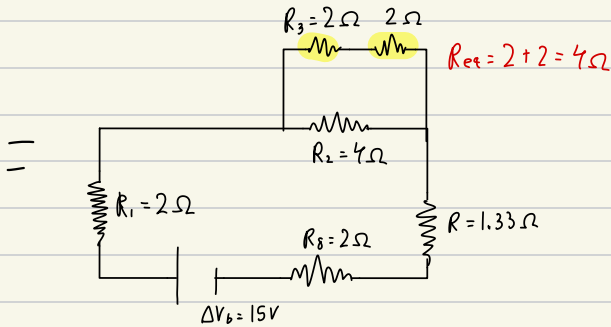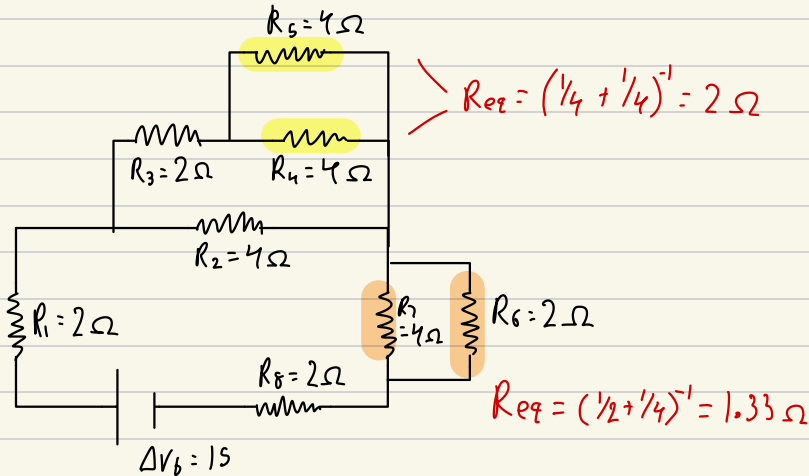Find equivalent resistance and total current, and current through and potential difference across each resistor in the circuit below.



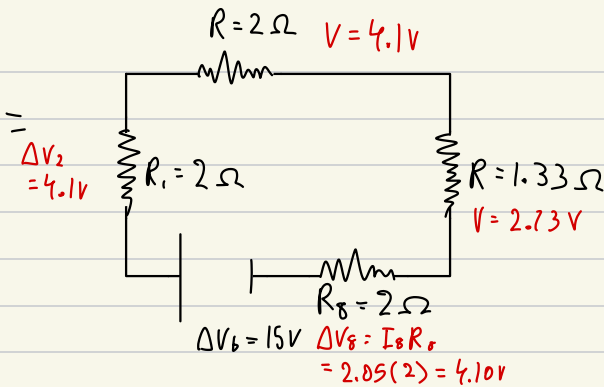

$$R_{eq} = 7.33\Omega$$

$$\Delta V_b = 15V$$

$$\Delta V_b = I_{tot} R_{eq}$$

$$15 = I_{tot} (7.33)$$

$$I_{tot} = 2.05A$$

$$I = \Delta V / R$$

* Go back & find vals

$$\Delta V_1 = 4.1V \quad I_1 = 2.05A$$

$$\Delta V_2 = 4.1V \quad I_2 = 1.025A$$

$$\Delta V_3 = 2.05V \quad I_3 = 1.025A$$

$$\Delta V_4 = 2.05V \quad I_4 = .6125A$$

$$\Delta V_5 = 2.05V \quad I_5 = .6125A$$

$$\Delta V_6 = 2.73V \quad I_6 = 1.365A$$

$$\Delta V_7 = 2.73V \quad I_7 = .6825A$$

$$\Delta V_8 = 4.1V \quad I_8 = 2.05A$$

Ex problem

A 30cm long copper wire is connected to a 250V power supply. An ammeter measures a current of 20mA passing through the wire. The resistivity of copper is $1,68 \times 10^{-8}$.

- a) Resistance of wire
- B) what is diameter of wire
- c) how much charge flows through wire in hour
- D) how many electrons pass
- E) how much energy dissipated in kwh

$$\Delta V = 250V$$

$$I = 20mA$$

$$\rho = 1,68 \times 10^{-8} \Omega m$$

$$l = 0,2m$$

$$a) \Delta V = IR$$

$$R = 250 / 20 \times 10^{-3} = \boxed{12500 \Omega}$$

$$b) R = \rho \frac{l}{A}$$

$$12500 = \frac{1,68 \times 10^{-8} (0,2)}{A}$$

$$A = 2,67 \times 10^{-13} m^2$$

$$A = \pi r^2 \rightarrow r = 2,93 \times 10^{-7} m$$

$$d = \boxed{5,86 \times 10^{-7} m}$$

$$c) I = Q/t$$

$$20 \times 10^{-3} = \frac{Q}{3600}$$

$$Q = 72C$$

$$d) \frac{72}{1,6 \times 10^{-19}} = 4,5 \times 10^{20} e^-$$

$$e) P = \Delta V I = 250 \times 20 \times 10^{-3} = 5W$$

$$P = E/t$$

$$5 = E/86400 \rightarrow$$

$$E = 432000J$$

$$kWh: P = 5W = 0,005kW$$


$$t = 24hr$$

$$E = Pt = 0,005 \times 24 = 0,12kWh$$

Capacitors and Circuits

Capacitance (C):

- Amount of charge it can hold

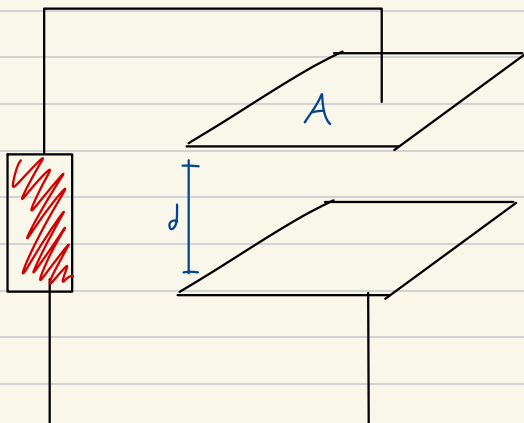

$$C = Q/\Delta V$$

*Always keeps the same proportion
Measured in Farads (F)

$$\vec{E} = \frac{\sigma}{\epsilon_0}$$

$\sigma \rightarrow$ Charge/unit area on a plate of capacitor

$$\sigma = Q/A$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$

$$C = Q/\Delta V$$

$$C = \frac{\epsilon_0 A}{d}$$

$$\vec{E} = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

$$\Delta V_c = \frac{Q d}{A \epsilon_0}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$

$$\vec{E} = \frac{\Delta V_c}{\Delta x} = \frac{\Delta V_c}{d}$$

$$\frac{\sigma}{\epsilon_0} = \frac{\Delta V_c}{d}$$

$$\Delta V_c = \frac{\sigma(d)}{\epsilon_0}$$

$$\Delta V_c = \frac{Q d/A}{\epsilon_0}$$


$$\Delta V_c = \frac{Q d}{A \epsilon_0}$$

$$C = Q/(Q d/A \epsilon_0) = \frac{\epsilon_0 A}{d}$$

Alt Formulas:

$$U_c = \frac{1}{2} Q V$$

$$U_c = \frac{1}{2} C \Delta V^2$$

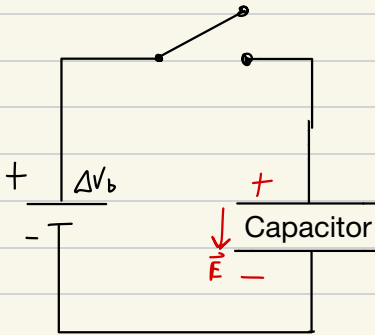

Asymptotic behavior:

- when the capacitor is initially uncharged, and just begins to charge (immediately after the switch is closed), **the capacitor acts like a bare wire (no resistance)(charge flows freely)**
- After the switch has been closed for a long time, **the capacitor is fully charged and acts like an open switch (no current flows in the circuit).**


Dielectric:

- An object you put in between the capacitor (ex. Insulator)
- The capacitor polarizes particles in the object causing an opposite E-field
- In other words a dielectric will weaken field of capacitor
- Has a dielectric strength (max E-field before it breaks down)

$\epsilon \rightarrow$ Permittivity of dielectric


Dielectric const. $k = \frac{\epsilon}{\epsilon_0}$

$$C = \epsilon \frac{A}{d} \quad || \quad C = k \epsilon_0 \frac{A}{d}$$

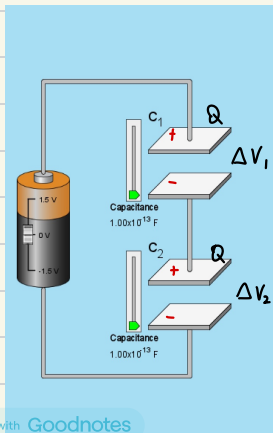

$$\Delta V_b = \Delta V_1 + \Delta V_2$$


Series

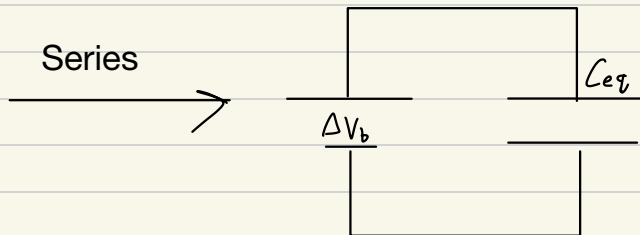


$$C_{eq} = \frac{Q}{\Delta V_b} \rightarrow \Delta V_b = \frac{Q}{C_{eq}}$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2} \rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$
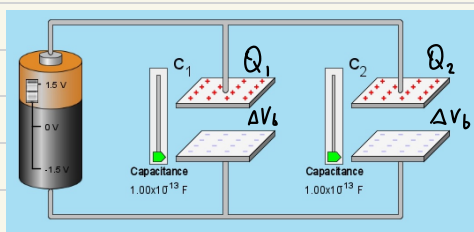
$$\frac{1}{C_{eq}} = \sum_{i=1}^n \frac{1}{C_i}$$



Parallel

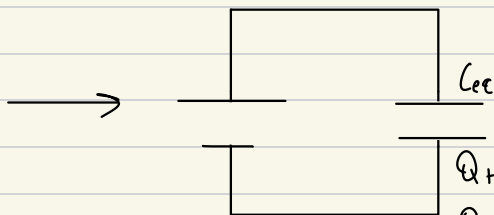

$$Q_{tot} = Q_1 + Q_2$$

$$Q_{tot} = C_{eq} \Delta V_b$$


$$Q_{tot} = C_1 \Delta V_1 + C_2 \Delta V_2$$

$$C_{eq} \Delta V_b = \Delta V_b (C_1 + C_2)$$

$$C_{eq} = C_1 + C_2$$

$$C_{eq} = \sum_{i=1}^n C_i$$

Quick Overview:

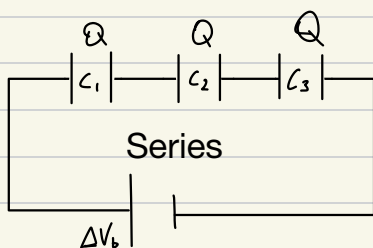


Series

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

$$\Delta V_b = \Delta V_1 + \Delta V_2 + \Delta V_3$$

$$C = Q / \Delta V$$

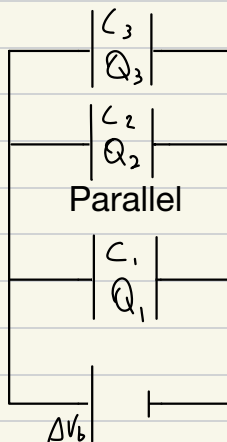


Parallel

$$C_{eq} = C_1 + C_2 + C_3$$

$$\Delta V_1 = \Delta V_2 = \Delta V_3$$

$$C = Q / \Delta V$$

Ex.

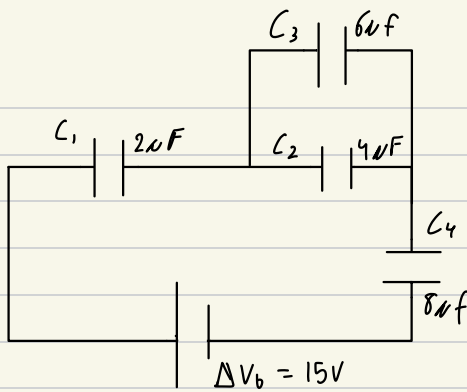

- Find equivalent capacitance of the combination
- Find individual potential difference and charge for each capacitor

$$a) C_{23} = C_2 + C_3 = 10\mu f$$

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_{23}} + \frac{1}{C_4} \right)^{-1} = 1.38\mu f$$

$$b) Q_{tot} = C_{eq} \Delta V = 20.7\mu C$$

$$Q_1 = Q_{23} = Q_4 = 20.7\mu C$$

$$\Delta V_1 = Q_1 / C_1 = \frac{20.7}{2} = 10.35V$$

$$\Delta V_4 = Q_4 / C_4 = \frac{20.7}{8} = 2.59V$$


$$\Delta V_{23} = Q_{23} / C_{23} = \frac{20.7}{10} = 2.07V$$

$$\Delta V_2 = \Delta V_3 = \Delta V_{23} = 2.07V$$


$$Q_2 = \Delta V_2 C_2 = 2.07(4) = 8.28\mu C$$

$$Q_3 = \Delta V_3 C_3 = 2.07(6) = 12.42\mu C$$



Ex.

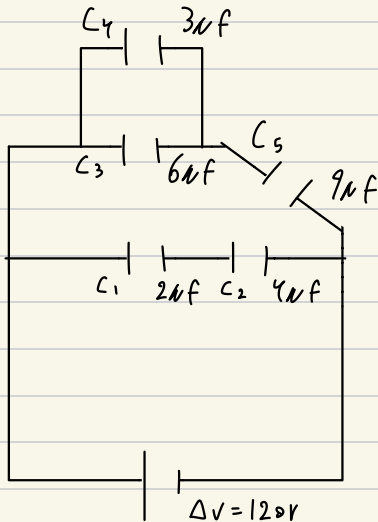

≡

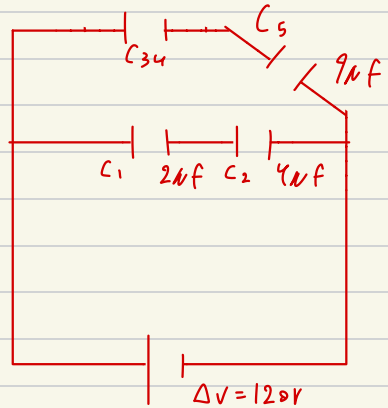

$$C_{34} = C_3 + C_4 = 6 + 3 = 9 \mu f$$

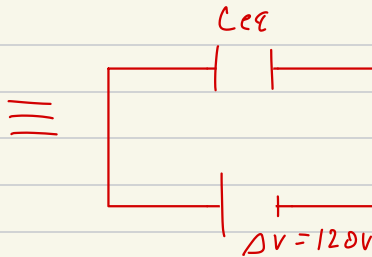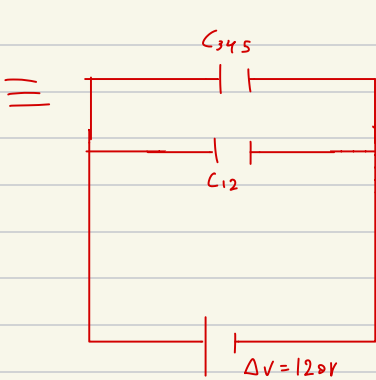

$$C_{345} = \left(\frac{1}{C_{34}} + \frac{1}{C_5} \right)^{-1} = 4.5 \mu f$$

$$C_{12} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = 1.33 \mu f$$

$$C_{eq} = C_{345} + C_{12} = 5.83 \mu f$$

$$Q_{tot} = C_{eq} (\Delta V) = 699.6 \mu C$$

$$\Delta V_{12} = \Delta V_{345} = 120V$$

$$Q_{12} = C_{12} \Delta V_{12} = 159.6 \mu C$$

$$Q_{345} = C_{345} \Delta V_{345} = 540 \mu C$$

$$Q_{12} = Q_1 = Q_2 = 159.6 \mu C$$

$$Q_{34} = Q_5 = 540 \mu C$$

$$\Delta V_{34} = \frac{Q_{34}}{C_{34}} = 60V$$

$$\Delta V_3 = \Delta V_4 = 60V$$

$$Q_3 = C_3 \Delta V_3 = 360 \mu C$$

$$Q_4 = C_4 \Delta V_4 = 180 \mu C$$

$$\Delta V_1 = \frac{Q_1}{C_1} = 79.8V$$

$$\Delta V_2 = \frac{Q_2}{C_2} = 39.9V$$

$$\Delta V_5 = \frac{Q_5}{C_5} = 60V$$


Kirchhoff's Rule:

Frequently, complex circuits cannot be reduced simply by using our understanding because of various reasons (ex. Not parallel or series)

- Kirchhoff's Rule is a tool to simplify circuits

Junction Rule:

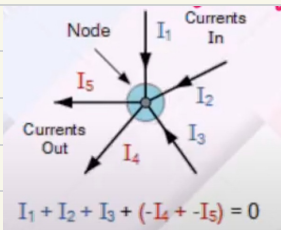- The sum of all currents entering a junction must equal sum of all currents leaving the junction



$$\sum I_{in} = \sum I_{out}$$


- Application of law of conservation of charge
- Current is flow of charge

Loop Rule:


- The sum of the changes in potential at different points around any closed circuit path or loop must be zero
- Application of conservation of energy
- In a closed loop, PE supplied by EMF must be transformed into other types of energy
- Sign Conventions:

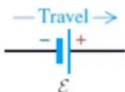(a) Sign conventions for emfs

+ $\mathcal{E}$: Travel direction from - to +:




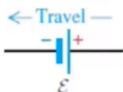- $\mathcal{E}$: Travel direction from + to -:




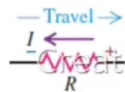(b) Sign conventions for resistors





+ IR : Travel *opposite* to current direction:




- IR : Travel *in* current direction:

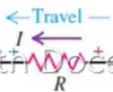


$$\sum \Delta V = 0$$

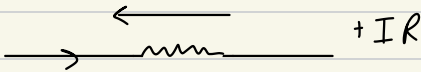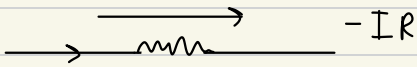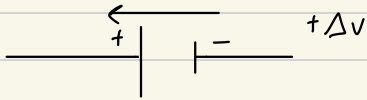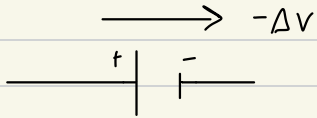

$-(E \Delta x)$

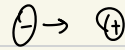


$\Delta V_E = +$

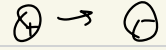

$\Delta V_E = -$



$\Delta V_E = -$

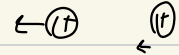


$\Delta V_E = +$

Batteries, Voltmeters and Ammeters

Internal resistance = Resistance of better

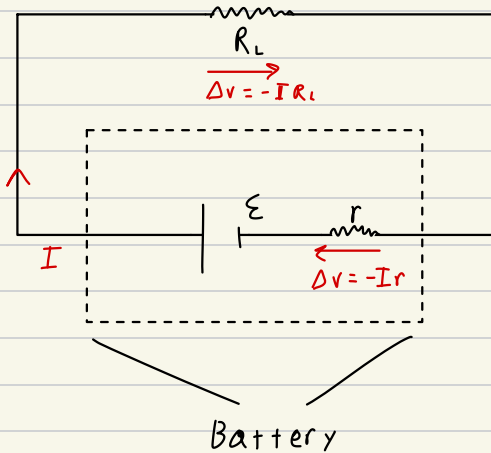- When electrons go through the battery they lose and gain energy



$\epsilon \rightarrow \text{emf} \rightarrow \text{Electromotive Force}$

$$R_{\text{eq}} = R_L + r$$

$$I = \frac{\epsilon}{R_{\text{eq}}} = \frac{\epsilon}{R_L + r}$$


Loop Rule:

$$\epsilon - IR_L - Ir = 0$$

$$\epsilon - Ir = IR_L \rightarrow \text{Terminal Voltage}$$


$$V_T = \epsilon - Ir$$

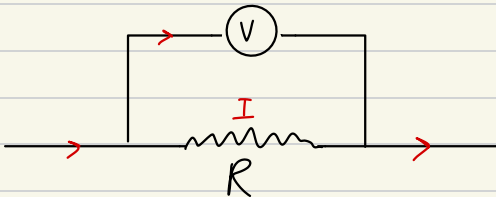- Ammeter connects in series because current needs to be same
- Voltmeter connects in parallel because voltage needs to be same





*Voltmeter must have a huge resistance to negate the fact that current splits (therefor changing the voltage)

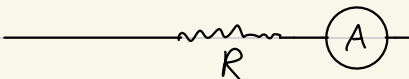- We want to limit the current that goes into the V-meter



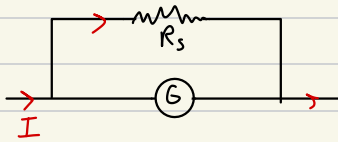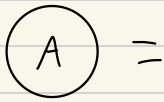*Similarly, ammeter must have a super low resistance to negate the current drop (due to resistance)



$$\Delta V_s = \Delta V_G$$

$$I_s R_s = I_G R_G$$


$$(I_{max} - I_s) R_s = I_G R_G$$

$$R_s = I_G R_G / (I_{max} - I_G)$$

$R_s = R$ -Shunt

G = Galvanometer (can only measure very small amounts of current)

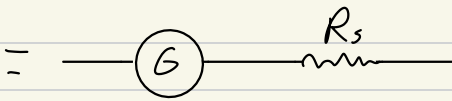Resistor put in place to not overload the galvanometer



$$\Delta V_{max} = \Delta V_G + \Delta V_s$$


$$= I_G R_G + I_G R_s$$

$$= I_G (R_G + R_s)$$

$$R_s = (\Delta V_{max} - I_G R_G) / I_G$$

- R_s is bigger

Capacitors and Resistors

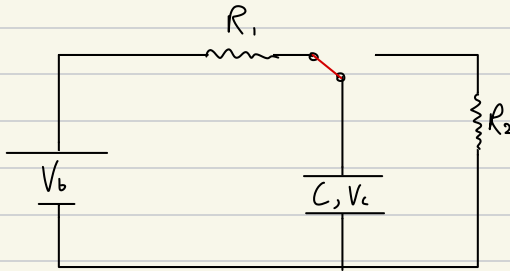

Loop Rule)

$$V_b - V_c - I R_1 = 0$$

$$V_b - \frac{Q}{C} - \frac{dQ}{dt} R_1 = 0$$

$$\frac{dQ}{dt} = \frac{V_b}{R_1} - \frac{Q}{R_1 C}$$

$$\left(\frac{dQ}{dt} = \frac{V_b}{R_1} - \frac{Q}{R_1 C} \right) dt$$

$$\frac{dQ}{dt} \cdot dt = \left(\frac{V_b}{R_1} - \frac{Q}{R_1 C} \right) dt \rightarrow \text{Time int.}$$

$$dQ = \left(\frac{V_b}{R_1} - \frac{Q}{R_1 C} \right) dt$$

$$\frac{dQ}{\left(\frac{V_b}{R_1} - \frac{Q}{R_1 C} \right)} = dt$$

At $t=0s$, $Q=0C$ (b/c the capacitor was uncharged before circuit activated)

$$\int \frac{dQ}{\left(\frac{V_b}{R_1} - \frac{Q}{R_1 C} \right)} = \int dt$$

$$u = \frac{V_b}{R_1} - \frac{Q}{R_1 C}$$

$$du = -\frac{dQ}{R_1 C}$$

$$-R_1 C du = dQ$$

$$\int \frac{-R_1 C du}{u} \rightarrow -R_1 C \int \frac{du}{u} = t + \eta$$

$$-R_1 C \ln(u) = t + \eta$$

$$\ln\left(\frac{V_b}{R_1} - \frac{Q}{R_1 C}\right) = \frac{-t}{R_1 C} - \frac{\eta}{R_1 C}$$

At $t=0$

$$\ln\left(\frac{V_b}{R_1}\right) = \frac{-\eta}{R_1 C} \rightarrow \eta = -R_1 C \ln\left(\frac{V_b}{R_1}\right)$$

$$\ln\left(\frac{V_b}{R_1} - \frac{Q}{R_1 C}\right) = \frac{-t}{R_1 C} + \frac{R_1 C \ln\left(\frac{V_b}{R_1}\right)}{R_1 C}$$

$$\ln\left(\frac{V_b}{R_1} - \frac{Q}{R_1 C}\right) = \frac{-t}{R_1 C} + \ln\left(\frac{V_b}{R_1}\right)$$

$$\ln\left(\frac{V_b}{R_1} - \frac{Q}{R_1 C}\right) - \ln\left(\frac{V_b}{R_1}\right) = \frac{-t}{R_1 C}$$

$$\ln\left(\frac{\frac{V_b}{R_1} - \frac{Q}{R_1 C}}{\frac{V_b}{R_1}}\right) = \frac{-t}{R_1 C} \quad (\text{Exponentiate to } e \text{ to get rid of } \ln)$$

$$\frac{\frac{V_b}{R_1} - \frac{Q}{R_1 C}}{\frac{V_b}{R_1}} = e^{\frac{-t}{R_1 C}}$$


$$\frac{V_b - \frac{Q}{R_1 C}}{R_1} = \frac{V_b}{R_1} e^{\frac{-t}{R_1 C}}$$

$$\frac{Q}{R_1 C} = \frac{V_b}{R_1} - \frac{V_b}{R_1} e^{\frac{-t}{R_1 C}}$$

$$Q = R_1 C \cdot \frac{V_b}{R_1} - R_1 C \cdot \frac{V_b}{R_1} e^{\frac{-t}{R_1 C}}$$

$$Q(t) = C V_b (1 - e^{\frac{-t}{R_1 C}})$$

$Q_{\max} = CV_b$

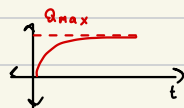

$$R_1 C = \tau \rightarrow$$

Time constant (bigger the time constant, the flatter the curve)

$t = \tau$ Time constant tells us how quick capacitor would charge

Charge:

$$Q(t) = Q_{max} (1 - e^{-\frac{t}{R_1 C}})$$
$$= Q_{max} (1 - e^{-1})$$

Voltage:

$$\Delta V(t) = \Delta V_b (1 - e^{-t/R_1 C})$$
$$V(t) = V_b (1 - e^{-t/R_1 C})$$


$$Q(t) = .632 Q_{max} \longleftrightarrow V(t) = .632 V_b$$

Current:


$$I(t) = \frac{dQ}{dt} = \frac{d}{dt} \left\{ Q_{max} (1 - e^{-t/R_1 C}) \right\}$$

$$I(t) = \frac{Q_{max}}{R_1 C} e^{-t/R_1 C}$$
$$= \frac{\Delta V_b}{R_1} e^{-t/R_1 C}$$

$$I(t) = \frac{V_b}{R_1} e^{-t/R_1 C}$$

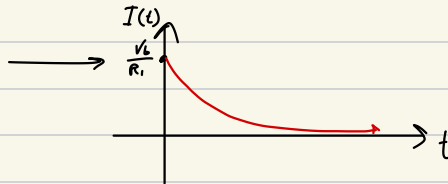


Flipped switch:

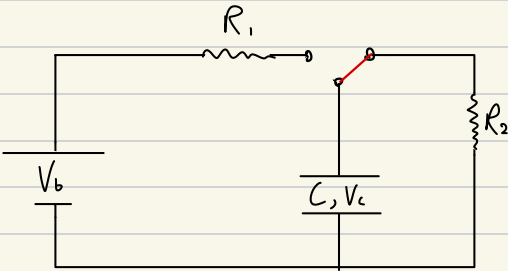

$$\begin{aligned}R_2 &= R \\V_c &= -V_R \\ \frac{Q}{C} &= -R \frac{dQ}{dt} \\ \frac{dQ}{dt} &= -\frac{Q}{RC} \\ \frac{dQ}{Q} &= -\frac{dt}{RC} \\ \int \frac{dQ}{Q} &= \int -\frac{dt}{RC}\end{aligned}$$

At $t=0$, $Q=Q_{\max}$
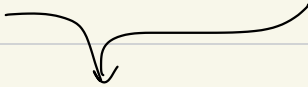
$$\begin{aligned}\int \frac{dQ}{Q} &= \int -\frac{dt}{RC} & \text{At } t=0: \\ \ln(Q) &= -\frac{t}{RC} + \eta & \ln(Q_{\max}) = \eta\end{aligned}$$




$$\ln Q = -\frac{t}{RC} + \ln Q_{\max}$$

$$\ln Q - \ln Q_{\max} = -\frac{t}{RC}$$

$$\ln(Q/Q_{\max}) = -t/RC$$

$$Q(t) = Q_{\max} e^{-t/RC}$$

Summary:

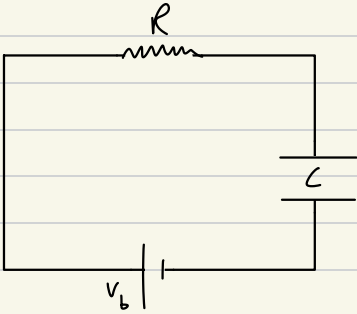

$$Q(t) = Q_{\max}(1 - e^{-t/RC}) \rightarrow \text{Charging}$$
$$V_C(t) = V_b(1 - e^{-t/RC})$$

$$Q(t) = Q_{\max} e^{-t/RC} \rightarrow \text{Discharging}$$

$$RC = \text{Time Constant} = \tau$$

At $t=0$, when circuit is just turned on, Q on capacitor is 0C

$$t=0, V_R = V_b \text{ \& } V_C = 0$$

$$t \rightarrow \infty, V_C = V_b \text{ \& } V_R = 0$$

Charging:

$$Q(\tau) = Q_{\max}(1 - e^{-1})$$
$$= .632 Q_{\max}$$

Discharge:

$$Q(t) = Q_{\max} e^{-t/RC}$$

$$Q(\tau) = Q_{\max}/e = .368 Q_{\max}$$

Energy of Capacitor: $E = \frac{1}{2}QV$ or $E = \frac{1}{2}CV^2$